

Lógica Digital (1001351)

Outros Circuitos Combinacionais



Prof. Ricardo Menotti

menotti@ufscar.br

Prof. Luciano de Oliveira Neris

lneris@ufscar.br

Atualizado em: 1 de abril de 2024

Departamento de Computação

Centro de Ciências Exatas e de Tecnologia

Universidade Federal de São Carlos

Comparadores

Comparador

 


Figure 4.22 A four-bit comparator circuit.

figure4.40.v

```
1 module compare (A, B, AeqB, AgtB, AltB);
2   input [3:0] A, B;
3   output reg AeqB, AgtB, AltB;
4
5   always @(A, B)
6   begin
7     AeqB = 0;
8     AgtB = 0;
9     AltB = 0;
10    if(A == B)
11      AeqB = 1;
12    else if (A > B)
13      AgtB = 1;
14    else
15      AltB = 1;
16  end
17
18 endmodule
```

Comparador por subtração

 


figure3.46.v

```
1 module comparator (X, Y, V, N, Z);
2   input [3:0] X, Y;
3   output V, N, Z;
4   wire [3:0] S;
5   wire [4:1] C;
6
7   fulladd stage0 (1'b1, X[0], ~Y[0], S[0], C[1]);
8   fulladd stage1 (C[1], X[1], ~Y[1], S[1], C[2]);
9   fulladd stage2 (C[2], X[2], ~Y[2], S[2], C[3]);
10  fulladd stage3 (C[3], X[3], ~Y[3], S[3], C[4]);
11  assign V = C[4] ^ C[3];
12  assign N = S[3];
13  assign Z = !S;
14
15 endmodule
16
17 module fulladd (Cin, x, y, s, Cout);
18   input Cin, x, y;
19   output s, Cout;
20
21   assign s = x ^ y ^ Cin,
22       Cout = (x & y) | (x & Cin) | (y & Cin);
23
24 endmodule
```

figure3.47.v

```
1 module comparator (X, Y, V, N, Z);
2   parameter n = 32;
3   input [n-1:0] X, Y;
4   output reg V, N, Z;
5   reg [n-1:0] S;
6   reg [n:0] C;
7   integer k;
8
9   always @(X, Y)
10 begin
11   C[0] = 1'b1;
12   for (k = 0; k < n; k = k + 1)
13   begin
14     S[k] = X[k] ^ ~Y[k] ^ C[k];
15     C[k+1] = (X[k] & ~Y[k]) | (X[k] & C[k]) | (~Y[k] & C[k]);
16   end
17   V = C[n] ^ C[n-1];
18   N = S[n-1];
19   Z = !S;
20 end
21
22 endmodule
```

Deslocadores

Deslocamento (*shift*)

 


Figure 4.50 A shifter circuit.

figure4.53.v

```
1 module shifter (W, Shift, Y , k);
2   input [3:0] W;
3   input Shift;
4   output reg [3:0] Y;
5   output reg k;
6
7   always @(W, Shift)
8   begin
9     if (Shift)
10    begin
11      Y[3] = 0;
12      Y[2:0] = W[3:1];
13      k = W[0];
14    end
15    else
16    begin
17      Y = W;
18      k = 0;
19    end
20  end
21
22 endmodule
```


figure4.54.v

```
1 module shifter (W, Shift, Y , k);
2   input [3:0] W;
3   input Shift;
4   output reg [3:0] Y;
5   output reg k;
6
7   always @ (W, Shift)
8   begin
9     if (Shift)
10    begin
11      Y = W >> 1;
12      k = W[0];
13    end
14    else
15    begin
16      Y = W;
17      k = 0;
18    end
19  end
20
21 endmodule
```

Deslocamento (*rotate*)

s_1	s_0	y_3	y_2	y_1	y_0
0	0	w_3	w_2	w_1	w_0
0	1	w_0	w_3	w_2	w_1
1	0	w_1	w_0	w_3	w_2
1	1	w_2	w_1	w_0	w_3

(a) Truth table

 

(b) Circuit

Figure 4.51 A barrel shifter circuit.

figure4.55.v

```
1 module barrel (W, S, Y);
2   input [3:0] W;
3   input [1:0] S;
4   output [3:0] Y;
5   wire [3:0] T;
6
7   assign {T, Y} = {W, W} >> S;
8
9 endmodule
```

ULA

Table 4.1 The functionality of the 74381 ALU.

Operation	Inputs $s_2\ s_1\ s_0$	Outputs F
Clear	0 0 0	0 0 0 0
$B - A$	0 0 1	$B - A$
$A - B$	0 1 0	$A - B$
ADD	0 1 1	$A + B$
XOR	1 0 0	$A \text{ XOR } B$
OR	1 0 1	$A \text{ OR } B$
AND	1 1 0	$A \text{ AND } B$
Preset	1 1 1	1 1 1 1

Table 4.1 The functionality of the 74381 ALU.

Operation	Inputs $s_2\ s_1\ s_0$	Outputs F
Clear	0 0 0	0 0 0 0
B-A	0 0 1	$B - A$
A-B	0 1 0	$A - B$
ADD	0 1 1	$A + B$
XOR	1 0 0	$A \text{ XOR } B$
OR	1 0 1	$A \text{ OR } B$
AND	1 1 0	$A \text{ AND } B$
Preset	1 1 1	1 1 1 1

```

1 // 74381 ALU
2 module alu (S, A, B, F);
3   input [2:0] S;
4   input [3:0] A, B;
5   output reg [3:0] F;
6
7   always @(S, A, B)
8     case (S)
9       0: F = 4'b0000;
10      1: F = B - A;
11      2: F = A - B;
12      3: F = A + B;
13      4: F = A ^ B;
14      5: F = A | B;
15      6: F = A & B;
16      7: F = 4'b1111;
17   endcase
18
19 endmodule

```

Verilog

Operadores em Verilog (1/2)

Table 4.2 Verilog operators.

Operator type	Operator symbols	Operation performed	Number of operands
Bitwise	~	1's complement	1
	&	Bitwise AND	2
		Bitwise OR	2
	\wedge	Bitwise XOR	2
	$\sim \wedge$ or $\wedge \sim$	Bitwise XNOR	2
Logical	!	NOT	1
	$\&\&$	AND	2
	\parallel	OR	2
Reduction	$\&$	Reduction AND	1
	$\sim\&$	Reduction NAND	1
		Reduction OR	1
	$\sim $	Reduction NOR	1
	\wedge	Reduction XOR	1
	$\sim\wedge$ or $\wedge \sim$	Reduction XNOR	1

Operadores em Verilog (2/2)

.			
Arithmetic	+	Addition	2
	-	Subtraction	2
	-	2's complement	1
	*	Multiplication	2
	/	Division	2
Relational	>	Greater than	2
	<	Less than	2
	>=	Greater than or equal to	2
	<=	Less than or equal to	2
Equality	==	Logical equality	2
	!=	Logical inequality	2
Shift	>>	Right shift	2
	<<	Left shift	2
Concatenation	{,}	Concatenation	Any number
Replication	{ {} }	Replication	Any number
Conditional	:?	Conditional	3


Precedencia dos Operadores em Verilog

Table 4.3 Precedence of Verilog operators.

Operator type	Operator symbols	Precedence
Complement	! ~ -	Highest precedence
Arithmetic	* / + -	
Shift	<< >>	
Relational	< <= > >=	
Equality	== !=	
Reduction	& ~& ^ ~^ ~	
Logical	&& 	
Conditional	:?	Lowest precedence


Erros comuns

Perigo!: Especificação Incompleta

 

```
1 module mux3to1(a, b, c, sel, out);
2   input [1:0] sel;
3   input a, b, c;
4   output out;
5   reg out;
6
7   always @(a or b or c or sel)
8   begin
9     case (sel)
10       2'b00: out = a;
11       2'b01: out = b;
12       2'b10: out = c;
13     endcase
14   end
15 endmodule
```

Perigo!: Especificação Incompleta

 


Evitando a Especificação Incompleta

```
1  always @(a or b or c or sel)
2    begin
3      out = 1'bx
4      case (sel)
5        2'b00: out = a;
6        2'b01: out = b;
7        2'b10: out = c;
8      endcase
9    end
```

```
1  always @(a or b or c or sel)
2    begin
3      case (sel)
4        2'b00: out = a;
5        2'b01: out = b;
6        2'b10: out = c;
7        default: out = 1'bx
8      endcase
9    end
```


Perigo!: Prioridade Indesejada

 


$I_3\ I_2\ I_1\ I_0$	$E_1\ E_0$
0 0 0 1	0 0
0 0 1 0	0 1
0 1 0 0	1 0
1 0 0 0	1 1
all others	XX

```
1 module binary_encoder(i, e);
2   input [3:0] i;
3   output [1:0] e;
4   reg e;
5
6   always @(i)
7   begin
8     if (i[0])
9       e = 2'b00;
10    else if (i[1])
11      e = 2'b01;
12    else if (i[2])
13      e = 2'b10;
14    else if (i[3])
15      e = 2'b11;
16    else
17      e = 2'bxx;
18  end
19 endmodule
```

Perigo!: Prioridade Indesejada

 

Evitando Prioridade Indesejada

 

```
1 module binary_encoder(i, e);
2   input [3:0] i;
3   output [1:0] e;
4   reg e;
5
6   always @(i)
7   begin
8     if (i == 4'b0001)
9       e = 2'b00;
10    else if (i == 4'b0010)
11      e = 2'b01;
12    else if (i == 4'b0100)
13      e = 2'b10;
14    else if (i == 4'b1000)
15      e = 2'b11;
16    else
17      e = 2'bxx;
18  end
19 endmodule
```

Bibliografia

Bibliografia

- Brown, S. & Vranesic, Z. - Fundamentals of Digital Logic with Verilog Design, 3rd Ed., Mc Graw Hill, 2009

Lógica Digital (1001351)

Outros Circuitos Combinacionais



Prof. Ricardo Menotti

menotti@ufscar.br

Prof. Luciano de Oliveira Neris

lneris@ufscar.br

Atualizado em: 1 de abril de 2024

Departamento de Computação

Centro de Ciências Exatas e de Tecnologia

Universidade Federal de São Carlos