

Lógica Digital (1001351)

Circuitos Sequenciais: Latches e Flip-flops



Prof. Ricardo Menotti

menotti@ufscar.br

Prof. Luciano de Oliveira Neris

lneris@ufscar.br

Atualizado em: 1 de abril de 2024

Departamento de Computação

Centro de Ciências Exatas e de Tecnologia

Universidade Federal de São Carlos

Circuitos Sequenciais

Nesta aula vamos aprender sobre:

- Circuitos lógicos que podem armazenar informações;
- Latches e Flip-flops, os quais armazenam um único bit.

 


Figure 5.1 Control of an alarm system.


 


Figure 5.2 A simple memory element.


Latch básico

 


(a) Circuit

S	R	Q_a	Q_b	
0	0	0/1	1/0	(no change)
0	1	0	1	
1	0	1	0	
1	1	0	0	

(b) Characteristic table

 


Latch com habilita (*gated latch*)

 

(a) Circuit


Clk	S	R	$Q(t+1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(b) Characteristic table

 


(c) Timing diagram

Latch com habilita (*gated latch*)

 

(c) Timing diagram

 

(d) Graphical symbol

Figure 5.5 Gated SR latch.

Latch construído com portas NAND


 


Figure 5.6 Gated SR latch with NAND gates.


Latch D

 

(a) Circuit


Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

 

(c) Graphical symbol


Latch D

 


(d) Timing diagram

Figure 5.7 Gated D latch.

Flip-flop D Mestre/Escravo

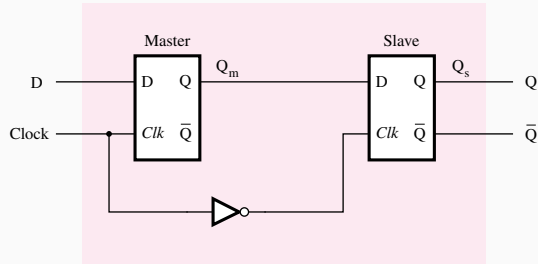


(a) Circuit

 


(b) Timing diagram

Flip-flop D Mestre/Escravo

 


(b) Timing diagram

 


(c) Graphical symbol

Figure 5.9 Master-slave D flip-flop.

Flip-flop D com borda positiva (subida)

 


(a) Circuit

 


(b) Graphical symbol

Figure 5.11 A positive-edge-triggered D flip-flop.

 Flip-flop D Mestre/Escravo com Clear e Preset




(a) Circuit

 


(b) Graphical symbol

Figure 5.12 Master-slave D flip-flop with *Clear* and *Preset*.

 
Flip-flop D Mestre/Escravo com borda positiva



(a) Circuit

 


Flip-flop T

 


(a) Circuit

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

(b) Characteristic table

 


(c) Graphical symbol

 

(d) Timing diagram


Figure 5.15 T flip-flop.

Flip-flop JK

 

(a) Circuit

J	K	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$\bar{Q}(t)$

 

- Brown, S. & Vranesic, Z. - Fundamentals of Digital Logic with Verilog Design, 3rd Ed., Mc Graw Hill, 2009
- <https://www.falstad.com/circuit/e-nandff.html>

Lógica Digital (1001351)

Circuitos Sequenciais: Latches e Flip-flops



Prof. Ricardo Menotti

menotti@ufscar.br

Prof. Luciano de Oliveira Neris

lneris@ufscar.br

Atualizado em: 1 de abril de 2024

Departamento de Computação

Centro de Ciências Exatas e de Tecnologia

Universidade Federal de São Carlos